

Lab 1 Report

Digital-Analog Converter

By Ogbonnaya Okorie

Goal

Design a 5-bit R-2R ladder digital-to-analog converter (DAC).

Procedure

Drew up a schematic of a R-2R divider circuit that will be used as a base for our DAC.

 


Figure 1.1: R-2R Divider

- Figure 1.2 displays the icon view of the R-2R divider, and the icon view that will be simulated

 


Figure 1.2: R-2R Divider Base & Sim Icon View

- Figure 1.3 displays the operating point of the R-2R divider with a voltage source of 5V.

```
*** SPICE deck for cell r_divider_sim[sch] from library lab_1_dac

--- Operating Point ---

V(vin):      1      voltage
V(vout):     0.333333 voltage
I(Vin):      -3.33333e-005 device_current
Ix(r_divide@0:BOT): -3.33333e-005 subckt_current
Ix(r_divide@0:IN):  3.33333e-005 subckt_current
Ix(r_divide@0:OUT): 0      subckt_current
```

Figure 1.3: R-2R Operating Point Schematic Results

- Figure 1.4 is the layout of the 10k n-well resistors in its serpentine shape to replicate the R-2R divider.
 - The 10k n-well resistor has a width of 14 and a length of 164. These values were picked based on the rough estimate of $R_{\text{square}} = 855 \text{ ohms/square}$.
 - 10,000 ohms divided by 855 ohms/square was roughly 11.7.
 - The minimum n-well width must be 12 - I picked 14. Multiplying 14 by 11.7 gave me 163.7; I rounded up to 164.
- Figure 1.5 is the operating point results of the layout.

 


Figure 1.4: Layout of R-2R Divider

```

*** SPICE deck for cell r_divider_sim{lay} from library lab_1_dac

--- Operating Point ---

V(vin):      1          voltage
V(vout):     0.333333   voltage
I(Vin):      -3.33333e-005 device_current
Ix(r_divide@0:BOT):  -3.33333e-005 subckt_current
Ix(r_divide@0:IN):   3.33333e-005 subckt_current
Ix(r_divide@0:OUT):  0          subckt_current

```

Figure 1.5: R-2R Operating Point Layout Results

 


Figure 1.6: 3D Layout View of R-2R Divider

To construct the DAC, I cascade the R-2R divider in a 5-bit ladder, also adding another 10k ohm resistor in series at the ground.

- For an ideal R-2R ladder, if all resistances are the same, the output resistance of the DAC is R. In this case R is 10k ohms; so the output resistance of the DAC is 10k ohms.

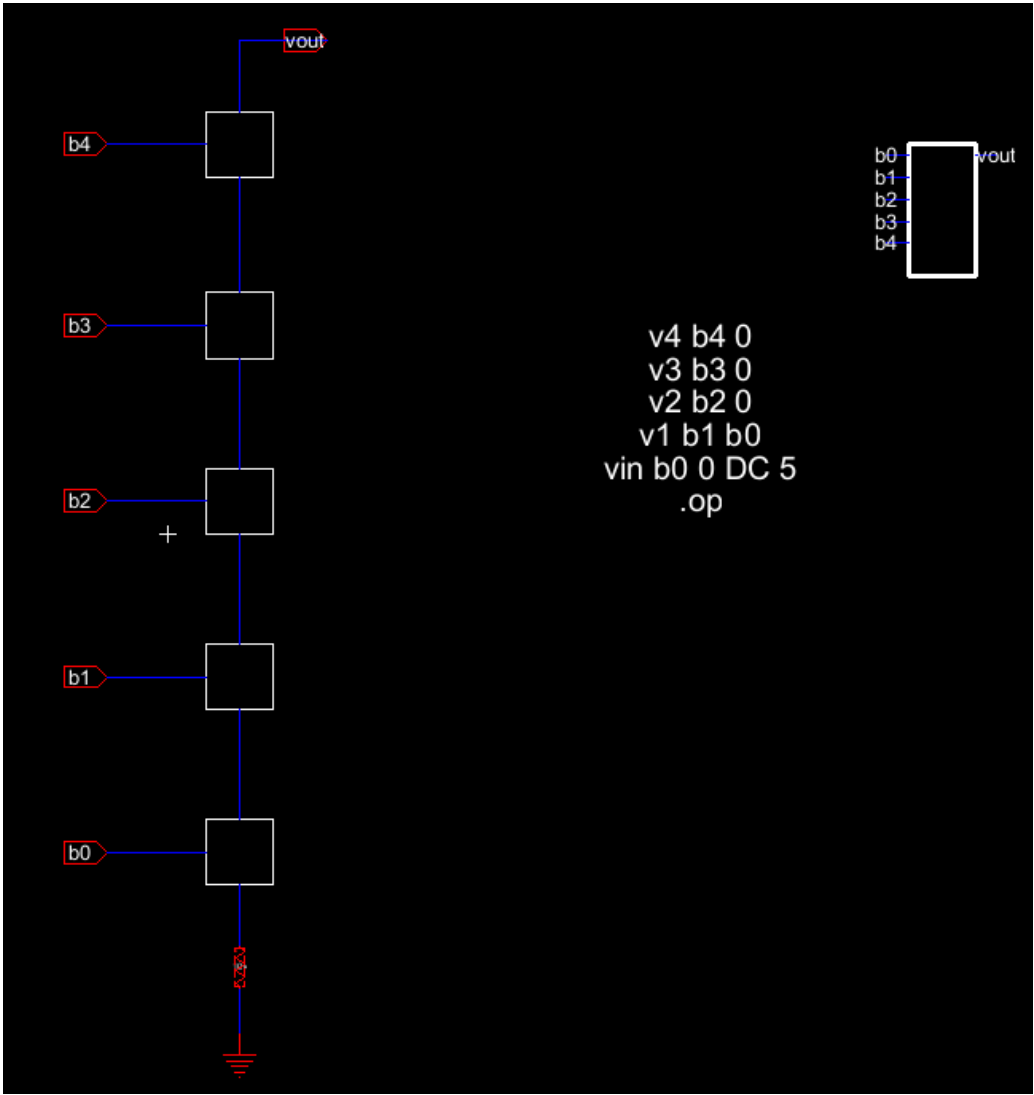


Figure 2.1: DAC Schematic

- Figure 2.2 displays the icon view of the DAC.

 


Figure 2.2: DAC Icon View

- Figure 2.3 displays the operating point of the DAC with a voltage source of 5V.

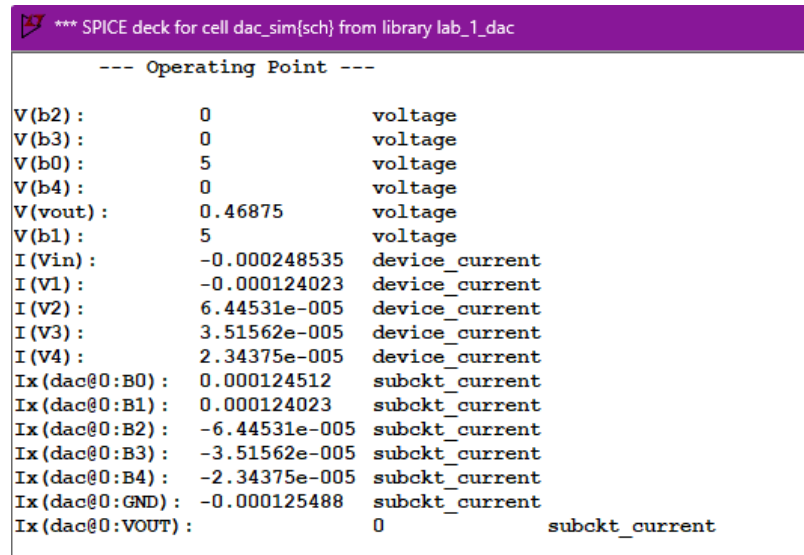


Figure 2.3: DAC Operating Point Schematic Results

- Figure 2.4 is the layout of the DAC in its serpentine pattern. Figure 2.5 is the operating point results of the layout.

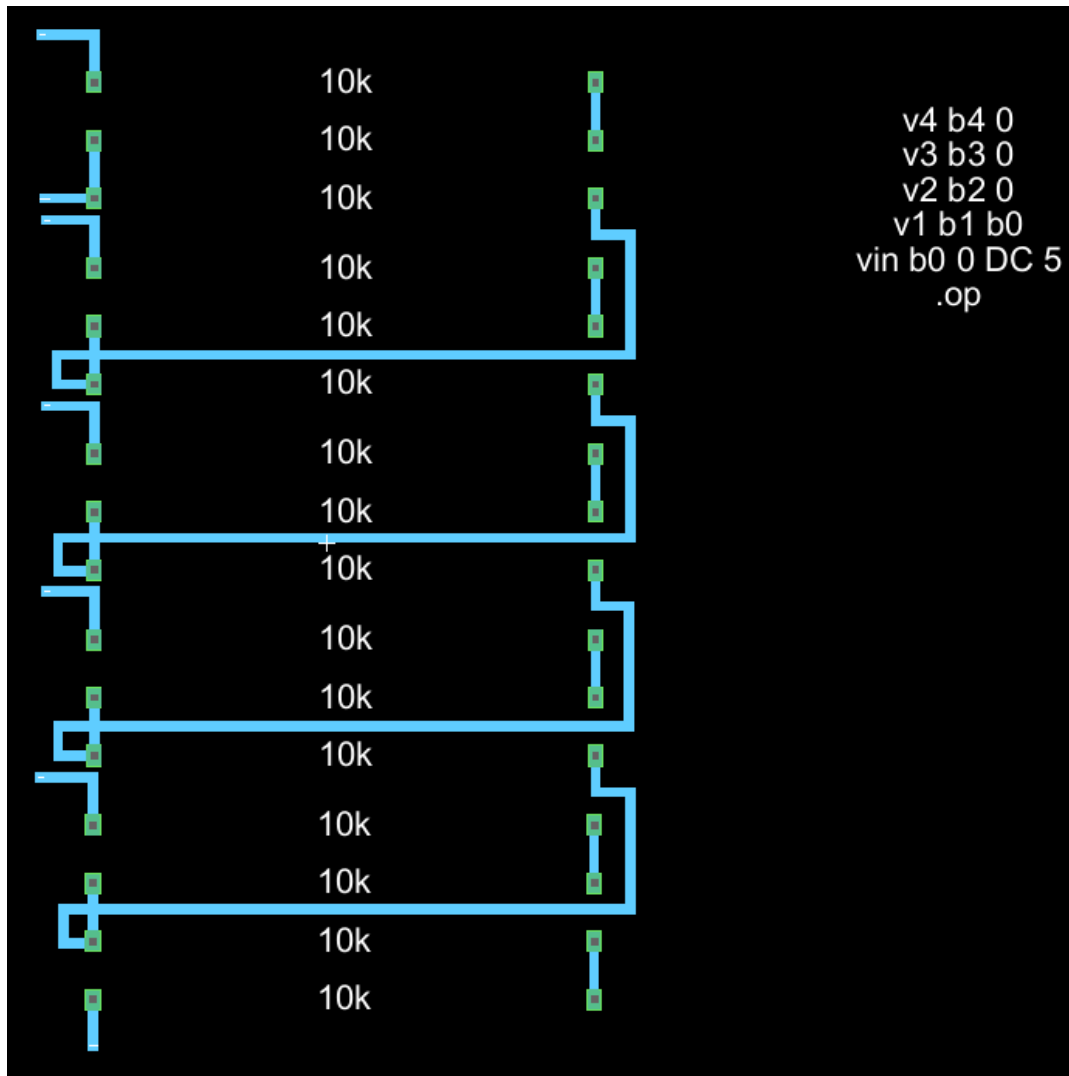


Figure 2.4: Layout of DAC

```
*** SPICE deck for cell dac_sim{lay} from library lab_1_dac

--- Operating Point ---

V(b4) :      0      voltage
V(vout) :    0.46875 voltage
V(b3) :      0      voltage
V(b2) :      0      voltage
V(b1) :      5      voltage
V(b0) :      5      voltage
I(Vin) :    -0.000248535 device_current
I(V1) :    -0.000124023 device_current
I(V2) :     6.44531e-005 device_current
I(V3) :     3.51562e-005 device_current
I(V4) :     2.34375e-005 device_current
Ix(dac@2:B0) : 0.000124512 subckt_current
Ix(dac@2:B1) : 0.000124023 subckt_current
Ix(dac@2:B2) : -6.44531e-005 subckt_current
Ix(dac@2:B3) : -3.51562e-005 subckt_current
Ix(dac@2:B4) : -2.34375e-005 subckt_current
Ix(dac@2:GND) : -0.000125488 subckt_current
Ix(dac@2:VOUT) : 0      subckt_current
```

Figure 2.5: DAC Operating Point Layout Results

- Figure 2.6 is the 3D layout of the DAC.

 


Figure 2.6: 3D Layout View of DAC

- Figure 3.1 displays the DAC schematic and icon where all of bits 0-3 are grounded, but bit 4 has an input voltage of 5V.
 - Figure 3.2 is the operating point of the grounded DAC schematic.

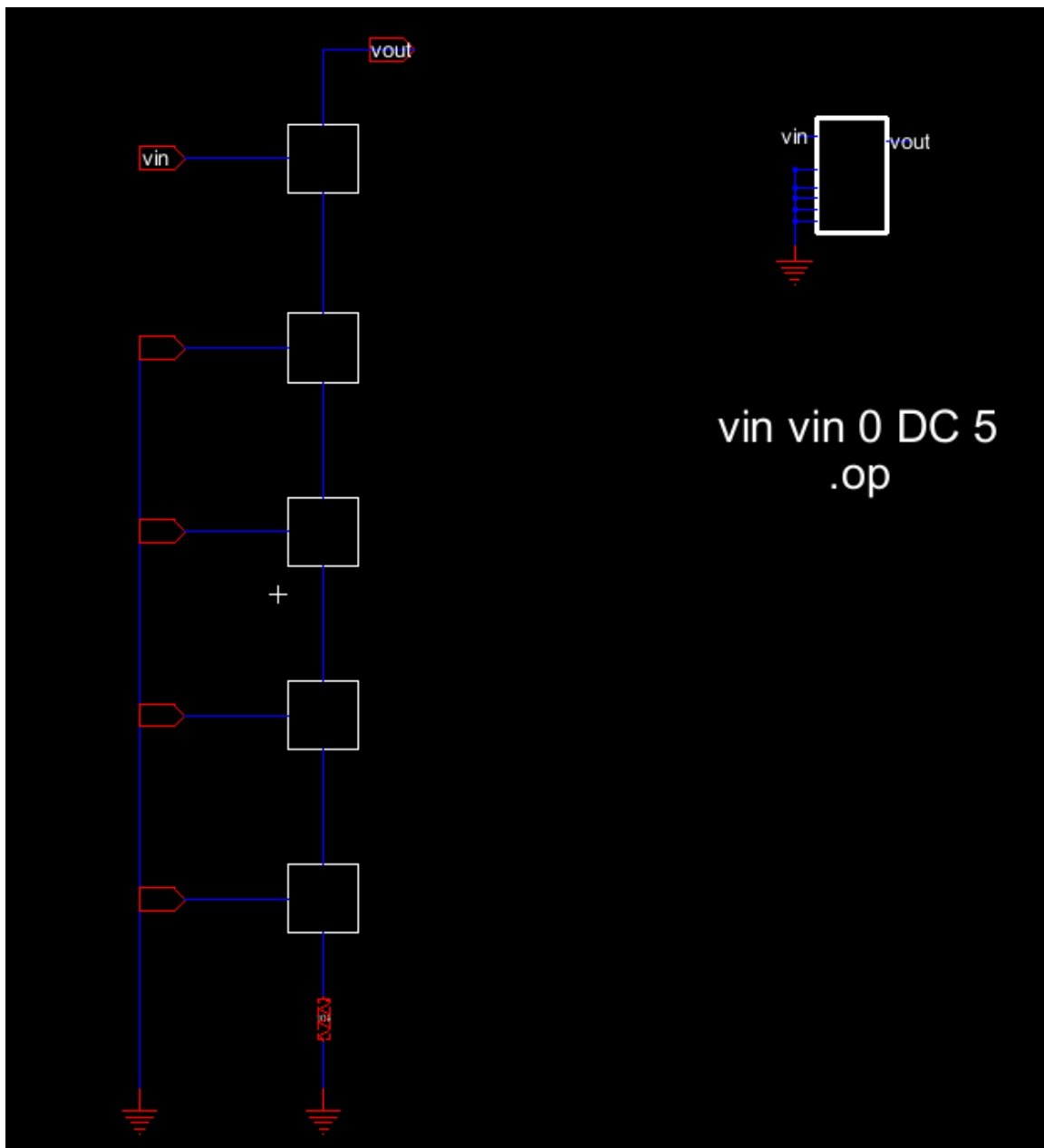


Figure 3.1: Grounded DAC Schematic & Icon

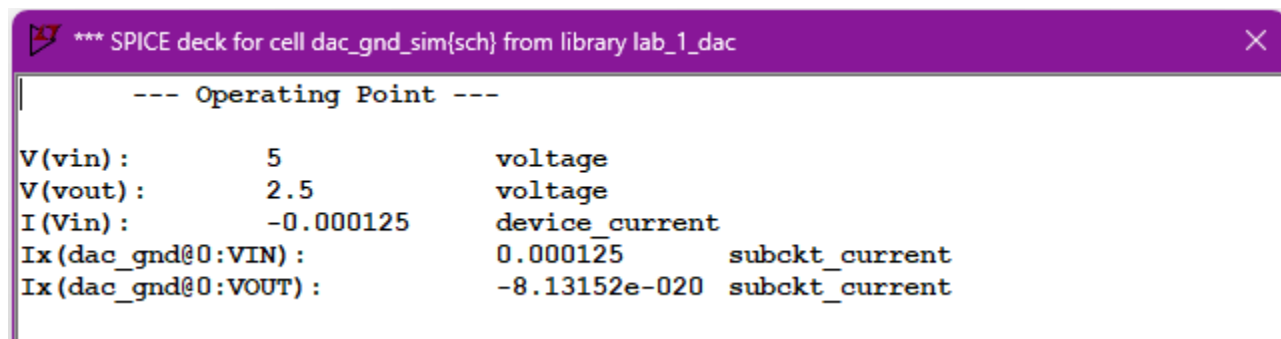


Figure 3.2: Grounded DAC Operating Points

- Figure 4.1 shows the grounded DAC schematic and icon with a 10 pF capacitor load.

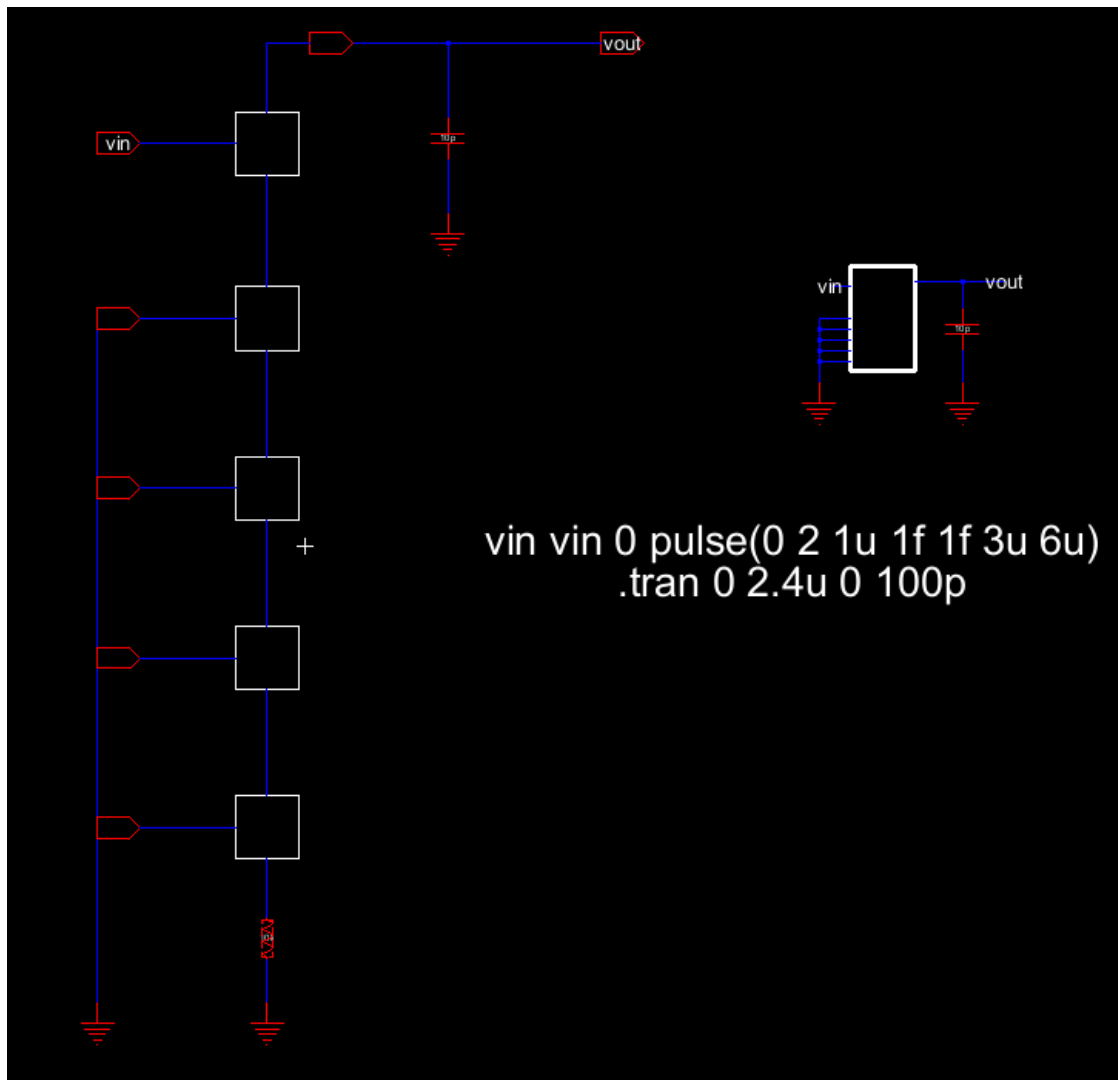


Figure 4.1: DAC with 10 pF Capacitor Load Schematic & Icon

- Figure 4.2 is a simulation of the capacitor at V_{out} being charged over time.
 - Hand calculations of the delay of the DAC is $0.7RC = (0.7)(10\text{kohms})(10\text{pf}) = 70\text{ns}$
 - Simulation observation agrees with hand calculations.

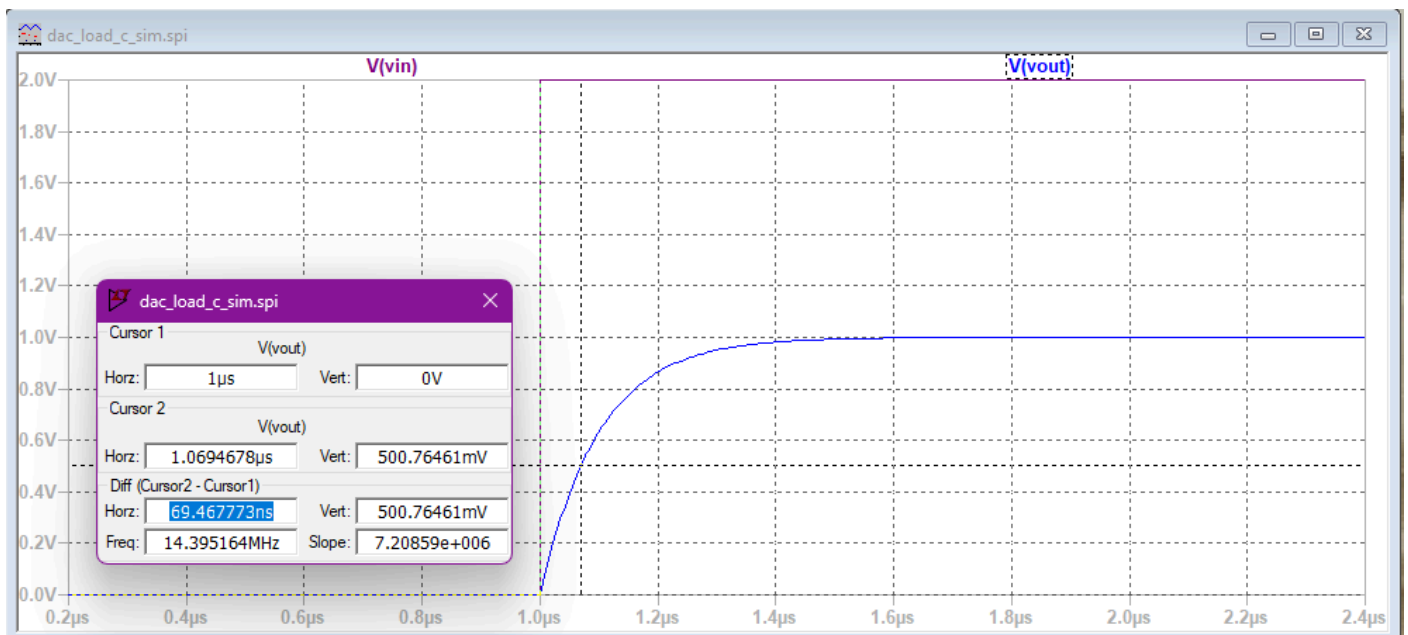


Figure 4.1: Simulation of DAC with 10 pF Capacitor Load

- Figure 5.1 shows the grounded DAC schematic and icon with a 10 pF capacitor and a 10k ohm load.
 - Adding a 10k ohm load changes the overall resistance of the DAC; the 10k ohm load is parallel to the 5-bit DAC, so the resistance changes as follows:
 - $$R = R_{DAC} \parallel R_{load} = (R_{DAC} * R_{load}) / (R_{DAC} + R_{load}) = (10k * 10k) / (10k + 10k) = 5k \text{ ohms}$$

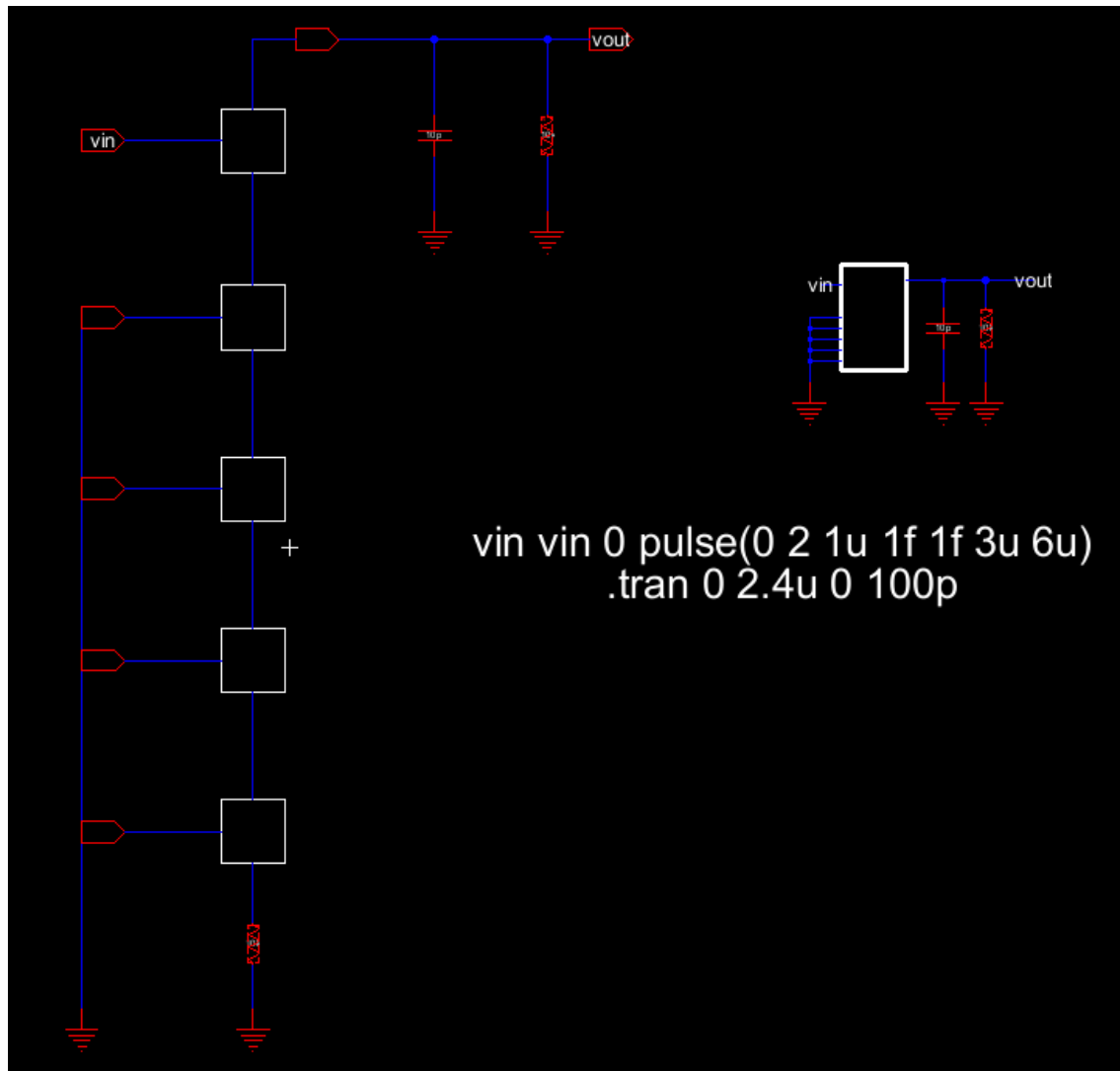


Figure 5.1: DAC with 10 pF Capacitor and 10k ohm Load Schematic & Icon

- Figure 5.2 is a simulation of the V_{out} being charged over time; the delay is halved from the previous schematic.
 - Hand calculations of the delay of the DAC is $0.7RC = (0.7)(5k\text{ohms})(10\text{pf}) = 35\text{ns}$
 - Simulation observation agrees with hand calculations.

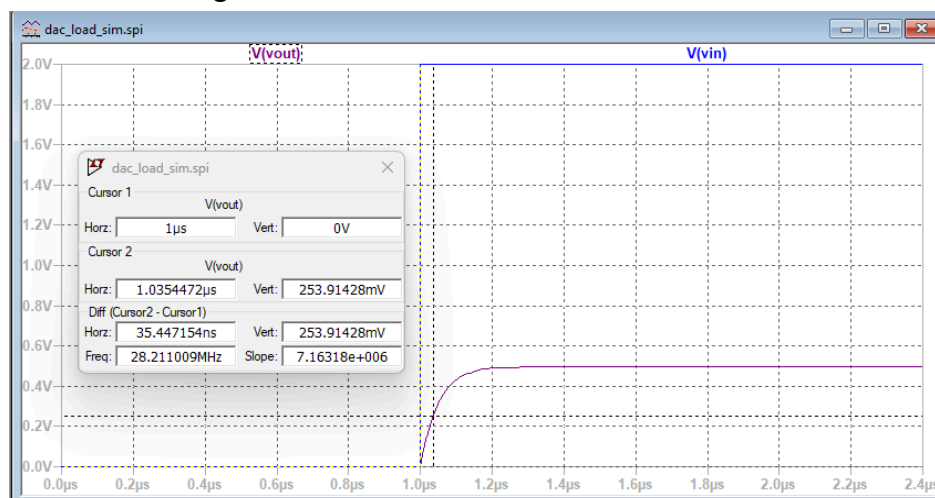


Figure 5.1: Simulation of DAC with 10 pF Capacitor and 10k ohm Load

DRC and LVS Check

```
Checking schematic cell 'r_divider{sch}'  
  No errors found  
Checking schematic cell 'dac{sch}'  
  No errors found  
Checking schematic cell 'dac_gnd{sch}'  
  No errors found  
Checking schematic cell 'dac_load{sch}'  
  No errors found  
Checking icon cell 'r_divider{ic}'  
  No errors found  
0 errors and 0 warnings found (took 0.001 secs)
```

Figure 6.1: DRC Check on DAC with Load

```
---  
Running DRC with area bit on, extension bit on, Mosis bit  
Checking again hierarchy .... (0.001 secs)  
Found 13 networks  
0 errors and 0 warnings found (took 0.003 secs)
```

Figure 6.2: LVS Check on DAC